



CAD ASSIGNMENT 1

EE476 DIGITAL INTEGRATED CIRCUIT DESIGN

Contributor: Gaohong Liu

Instructor: Visvesh Sathe, Naveen John

University of Washington

Department of Electrical Engineering


Table of Content

Procedure 1: IV Characteristics	2
Part a	2
Part b	3
Part c	5
Part d	5
Procedure 2: FET's with Resistances	7
Part a	7
Part b	8
Part c	8
Procedure 3: FET's as Resistances	9
Procedure 4: Gate Capacitance	9
Procedure 5: Additional Question	10
Part a	10
Part b	10
Part c	11
Part d	11
Part e	11

Procedure 1: IV Characteristics

 Part a

In part a, we are required find the iv characteristics of nmos with $w = 1\mu\text{m}$, and $l = 60\text{nm}$. In cadence, I just build circuit as required and I set one voltage source as 1.2 volts to V_{dd} and one voltage source as 1.2volts to V_g for my declaration. In order to get the plot of I_{ds} versus V_{gs} , I set up an DC analysis that V_{gs} can change from 0 volts to 1.2 volts, then I get plot of I_{ds} versus V_{gs} as below. It makes sense because when V_{gs} is larger than 0.2 which is approximately the threshold voltage, the nmos will turn on with below characteristics.




Part b

In part b, we are required the iv characteristics of nmos with two sets of V_{gate} , one is 0.6 volts and one is 1.2 volts. Because we want to plot of I_{ds} versus V_{ds} to get behavior of nmos within different operation region, we need execute a DC analysis that can change voltage across nmos. To achieve this, in my control file, I set up an voltage source as 1.2 to V_{dd} , and I connect


V_g to ground and gives it voltage as required, which is 0.6volts and 1.2volts separately. The waveforms below are my results.

For $V_g = 0.6v$

 

Under this situation, at the very beginning, the nmos is under cut off region, and then it enters triode region, and finally it stays in saturation region. When it enters saturation region, the V_{ds} is approximately equal to 0.4volts. It makes sense because V_{gs} equal to 0.6volts and V_{th} is approximately equal to 0.2volts.


For $V_g = 1.2v$

 

Under this situation, at the very beginning, the nmos is under cut off region, and then it enters triode region, and finally it stays in saturation region. When it enters saturation region, the V_{ds} is approximately equal to 1volts. It makes sense because V_{gs} equal to 1.2volts and V_{th} is approximately equal to 0.2volts.

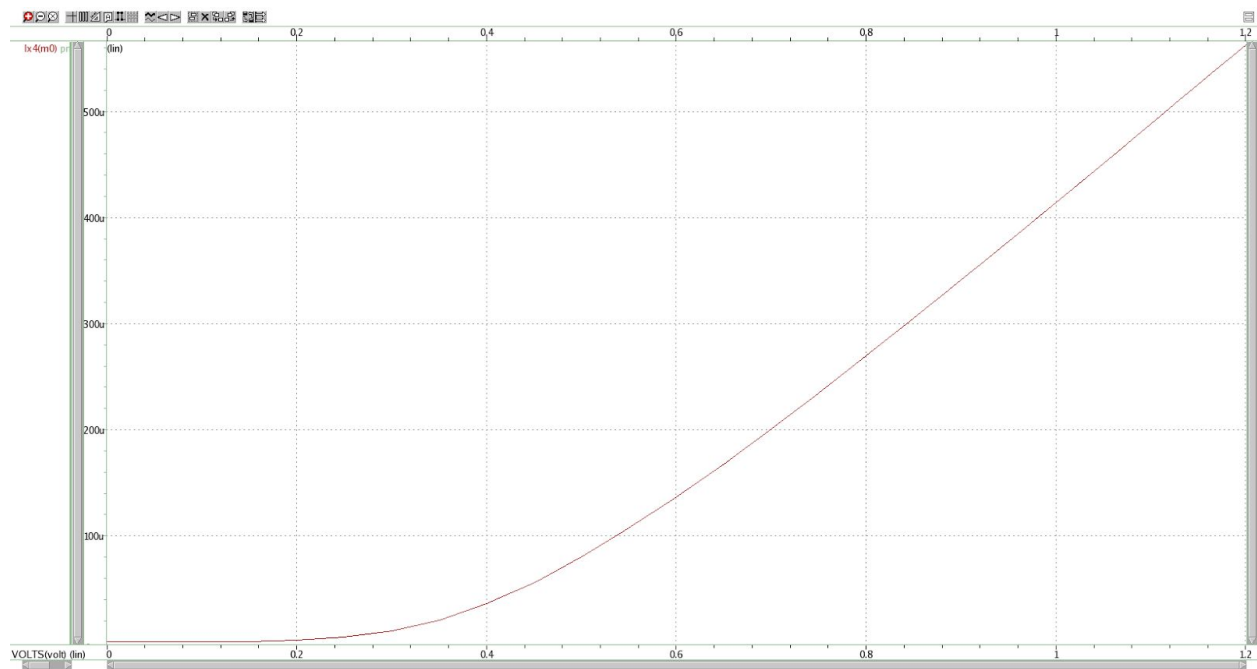Part c

In part C, we are required do the same thing to pmos as we did to nmos. The pmos we choose has $w = 1\mu m$, and $l = 60nm$ characteristics. I build the circuits as shown in specification. Because we need to find the iv characteristics that I_{sd} versus V_{sg} , so in my control file, I set voltage source V_{dd} as 1.2 and set up a DC analysis that I connect V_{dd} with V_g and the voltage between them can sweep from 0volt to 1.2volts. Then I got my result as below. This waveform is totally correct because when we increase V_{sg} , pmos then can turn on and then go to triode region until it becomes saturated.




Part d

In part d, we did the same thing to pmos as we did in part b. In order to see the behavior of pmos when it enters different operation regions, we need to find the waveform I_{sd} versus V_{sd} . Then we create two sets of V_g that 1.2volts and 0.6volts. In my control file, I set up two three voltage sources that one is V_g for gate voltage, one is V_{dd} which is 1.2volts and one is voltage supply that connects between pmos and ground which is used for make V_{gs} stable, and not change which V_{ds} . Then I set up a DC analysis that change voltage supply change from 1.2volts to 0volt because then we can have V_{sd} change from 0volt to 1.2 volts. Additionally, because set a DC analysis about V_{supply} , but we want waveform that about V_{sd} , I change my


waveform axis using built-in function that change my x axis to V_{sd} not V_{supply} , then I got my results as below.

For $V_g = 1.2v$

 

As shown in data, this pmos is always in cutoff region.

For $V_g = 0.6v$

 


As shown in waveform, the pmos is initially at cutoff region, and then it goes to triode region and finally it goes to saturation region. When it enters saturation, the V_{ds} approximately equals to 0.8

Procedure 2: FET's with Resistances

 
Part a

In part a, we are required find drain voltage of nmos with different resistor while changing the gate voltage from 0volt to 1.2volts. In my cadence set up, I build circuit required in specification without resistor connection. I did not connect resistor with Vdd and nmos transistor, and inversely, I leave them in schematic level without connect. However, in my control file I put resistor into DC analysis where resistor can change from 100k to 200k in one step, so I get two different resistor setting at one time. Additionally I put Vgate into DC analysis to change Vgate from 0volt to 1.2volts, and I set a voltage source at Vdd as 1.2volts. Then I got results as below.



 Part b


The basic setting is as same as part b. However, we need to change Vgate into a square wave voltage source where $T=500\text{ps}$, $T_{\text{rise}}=20\text{ps}$, and $T_{\text{fall}}=20\text{ps}$. Then I got below results.



Part c

In part c, we need to find the rise time and fall time of V_o with $r=100\text{k}\Omega$ in '.MEAS' and Measurement Tool ways. In .MEAS way, I just put .MEAS with rise time and fall time command. In .mt0 file where it contains my measurement results I got **rise_time=8.931e-11s** and **fall_time=3.973e-11s**. Using Measurement Tool, I choose fall time and rise time function, and enlarge the signal segment I want which are fall time part and rise time part. Then I result as following, where my measurement tool result is approximately equal to my .MEAS method

result, which means my results are reliable.

 

Procedure 3: FET's as Resistances


In procedure 3, we need to find resistance of nmos transistor. The basic idea is that I measure the current through the transistor and then use V_{ds} to divide by it and then I will get the corresponding resistance. So in my control file, I set a DC analysis of V_{dd} where it can jump from 25mv to 250mv at one time so I can get both resistance with different V_{ds} at same time. Then I set $V_{gate}=1.2$ volts as required. As for .MEAS command, I first ask it to FIND the current through transistor, and then I use .MEAS to use V_{ds}/I_{ds} , and so on the result stored in .ms0 file is the resistance as required.

In my .ms0, I get my results that when $V_{ds}=25mv$, $R=2.845e02\Omega$, and when $V_{ds}=250mv$, $R=3.090e02\Omega$.

Procedure 4: Gate Capacitance

In procedure 4, we need to find capacitance of gate. The basic idea is, we generate a pulse voltage, and then use .MEAS command to find the current through gate. After measurement, using waveform of current through gate and Function inside silicon explore to calculate charge through gate over time because $Q = \int i dt$. So I build circuit as described in specification, and use

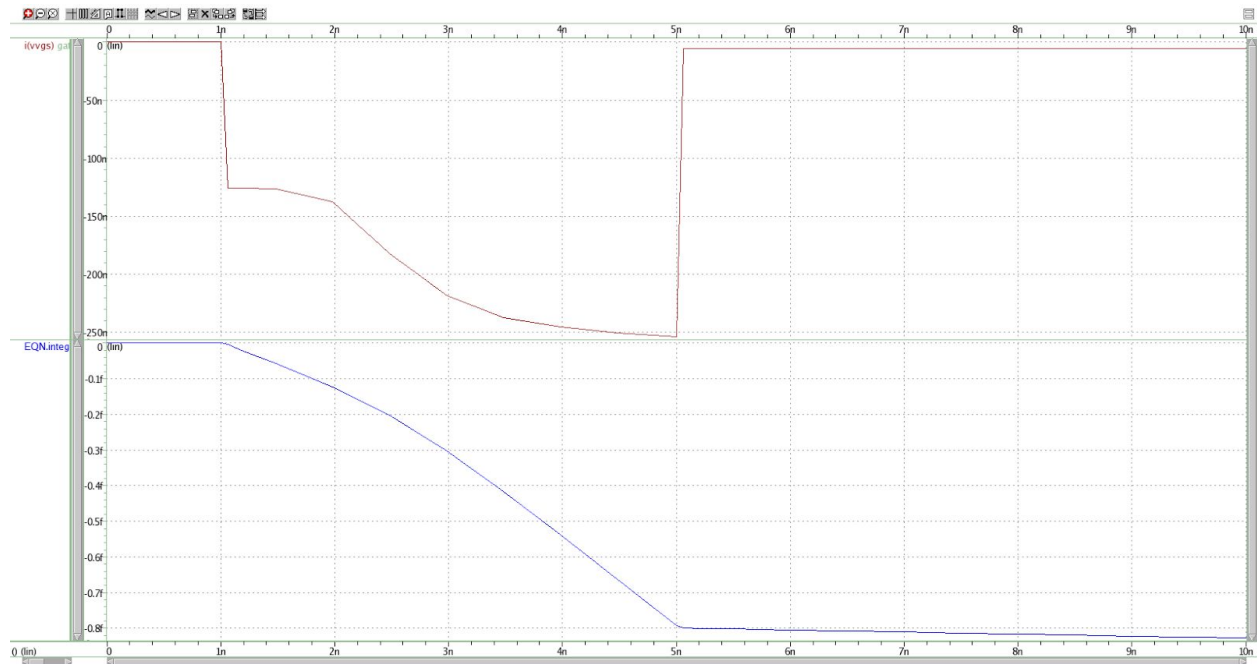PWL command to generate a pulse that in 1ps that the voltage across gate can increase from 0volt to 1volts and then use.MEAS command to calculate Q. In my .mt0 file I get $Q=-8.053e-16c$ and because $C=Q/V$, $c=8.053c/v$. To verify I get a reliable data, I use Measurement Tool's function to generate integral waveform and I got below result.



The total charge across gate is approximately equal to 0.8c so I get a reliable data in .mt0 file.

Procedure 5: Additional Question

Part a

In part a, I try to find V_{th} first. I locate saturation region in my waveform, and then I find the derivation line across that point. By finding the point that derivation line across x-axis, I got **$V_{th}=0.38volts$** . Then I locate two random points at saturation region. One is $V_1=1.19volts$, $I=1.1mA$, and one is $V_2=1.18volts$, $I=1.08mA$. I plug these data and V_{th} into function $I = \frac{1}{2}\beta(V_{gs} - V_{th})^n$, then I got a pair of equations. By dividing them, we can cancel β and get an equation about n . Solving it we get **$n=1.8$** . Finally plug back we get **$\beta=0.002241$**

Part b

Same procedure with part a, we get **$V_{th}=0.39volts$** , **$n=2.1375$** , and **$\beta=0.001142$** .
(Point1: $V_1=1.18volts$, $I_2=551uA$; Point2: $V_2=1.19volts$, $I_2=559uA$)

Part c

$$\frac{\beta_{nmos}}{\beta_{pmos}} = 1.9657$$

Part d

λ is the slope of the saturation region, so I simply use Measurement Tool in Silicon Explorer, the difference function to get slope. Then I get **$\lambda=271\mu \text{ A/V}$**

Part e

Same procedure in part d, I get **$\lambda=87\mu \text{ A/V}$**