



CAD ASSIGNMENT 4

EE476 DIGITAL INTEGRATED CIRCUIT DESIGN

Contributor: Gaohong Liu

Instructor: Visvesh Sathe, Naveen John

University of Washington

Department of Electrical Engineering

Part 6: Additional Question

a)

T_{cq} vs. T_{arrival}



b) 1.2v. Because comparing with 0.8v, 1.2v setting has smaller T_{cq}, which means lower delay, and smaller T_{setup} and T_{hold}, which means data can be stable within shorter time.

c) R+C+CC, because it has larger powerconsumption.

d) R+C+CC has larger resistance, larger rise time but smaller fall time. Circuit with or without load can have huge difference.